

Lecture 32

①

12 Nov 2014


Last time talked about LC

circuits

of how these
transfer electric

to magnetic energy

and back as an oscillator

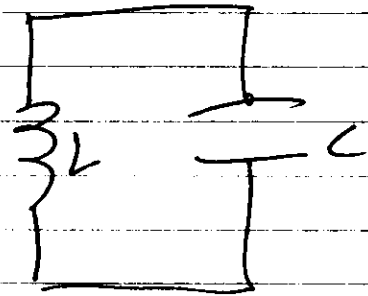

differential equation for circuit is

$$\frac{q(t)}{C} + L \frac{di(t)}{dt} = 0$$

$$\frac{di(t)}{dt} = \frac{d^2 q(t)}{dt^2}$$

found solutions to be

$$q(t) = Q \cos(\omega t + \phi)$$


$$\text{where } \omega = \frac{1}{\sqrt{LC}}$$

(2)

In reality, there is always some resistance, which leads to "damping" of oscillations (means that energy is decaying)


Before electric & magnetic energy go back & forth, but now this will be converted to thermal energy

circuit we consider is RLC

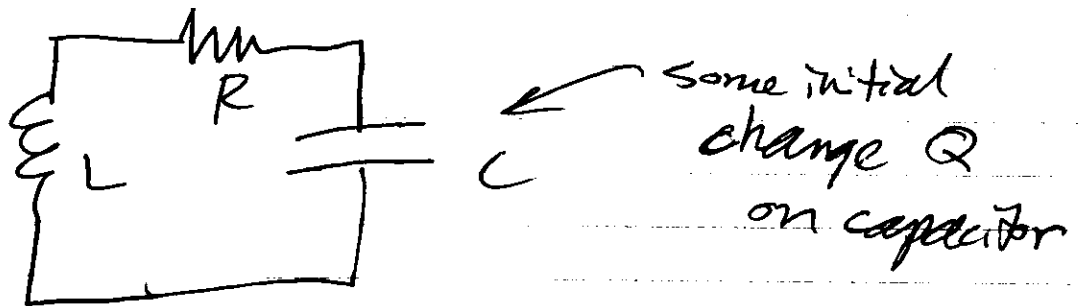

can solve the circuit in two ways:

QUESTIONS | loop rule

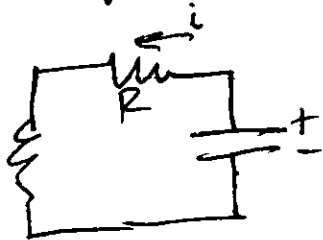

$$\frac{-q(t)}{C} - iR - L \frac{di(t)}{dt} = 0$$

3

$$\Rightarrow \frac{q(t)}{C} + \frac{dq(t)}{dt} R + L \frac{d^2q(t)}{dt^2} = 0$$

Solution to the diff. eq. is

$$q(t) = Q e^{-Rt/2L} \cos(\omega' t + \phi)$$

$$\text{where } \omega' = \sqrt{\omega^2 - (R/2L)^2}$$



$$\text{with } \omega = \frac{1}{\sqrt{LC}} \text{ (need } R \text{ small enough)}$$

check this solution yourself...

product of two terms


$$Q e^{-Rt/2L} \quad \&$$

$$\cos(\omega' t + \phi)$$

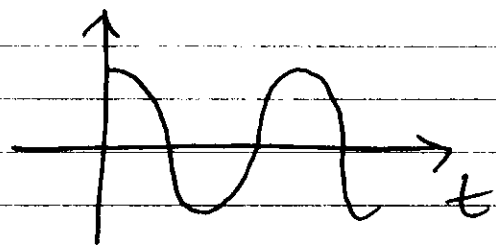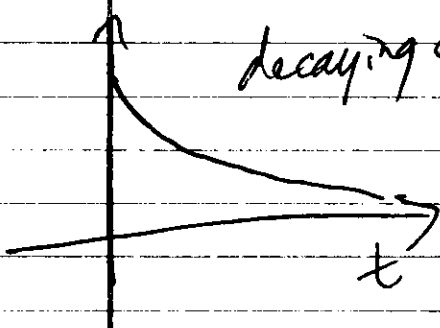

4

product then looks like

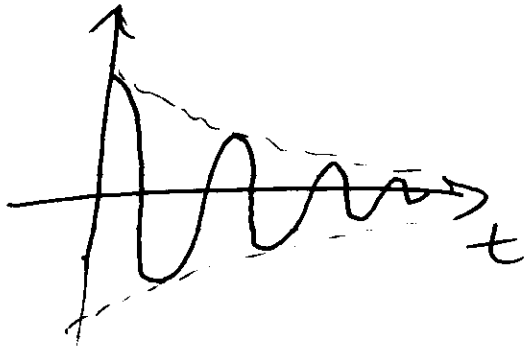

damped oscillations

Another way to get circuit equation:
use energy

Magnetic energy of inductor + electrical
energy
of cap. is

$$\frac{1}{2} L i^2 + \frac{1}{2C} q^2 = U$$

rate at which this decreases is
equal to power delivered to
~~the~~ resistor in
form of
thermal
energy

5

$$\Rightarrow -\frac{dU}{dt} = i^2 R$$

$$\Rightarrow -\frac{d}{dt} \left[\frac{1}{2} L i^2 + \frac{1}{2C} q^2 \right] = i^2 R$$

$$\Rightarrow \cancel{\frac{d}{dt} \left[\frac{1}{2} L i^2 + \frac{1}{2C} q^2 \right]} = i^2 R$$

$$-\frac{1}{2} L \cdot 2i \cdot \frac{di}{dt} - \frac{1}{2C} \cdot 2q \frac{dq}{dt} = i^2 R$$

$$\Rightarrow -L \frac{di}{dt} - \frac{q}{C} = iR$$

same equation

(6)

Alternating current -

oscillates back & forth w/ time

- much more practical for
the distribution of electrical
power over large distances

Why? For fixed power $P = VI$

can make voltage high or current high.

If current is high, then ^{much} more
power lost to heat $i^2 R$

But if voltage high, then less
is lost to heat V^2/R


Also it's easier to convert AC
from one voltage to another

(but it was more expensive &
inefficient to do w/ DC)

↳ and AC generators are cheaper
& more efficient

7

Model an AC generator as

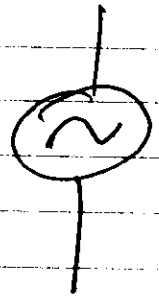

w/ EMF

$$\mathcal{E} = E_m \sin \omega t$$

↑ max EMF
↑ frequency of oscillation

current is then


$$i = I \sin(\omega t - \phi)$$

↑ phase ϕ is there
b/c current does not have to be in phase w/ EMF

three circuits to consider:

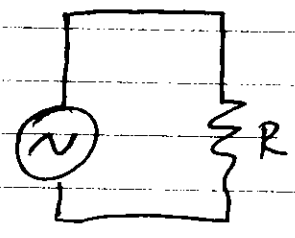QUESTION:

What is current through resistor if $\mathcal{E} = E_m \sin(\omega t)$?



8

$$\Rightarrow \text{current } i = \frac{E_m}{R} \sin(\omega t)$$


current is in phase w/ ^{AC} EMF

for purely resistive load.

Checkpoint:

If we increase frequency,
does amplitude of voltage &
current change?

Next circuit:

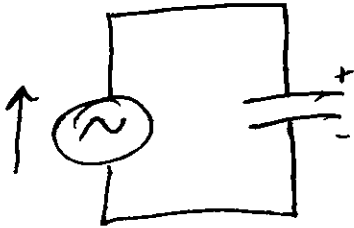

What is current?

use loop rule to get

$$E_m \sin(\omega t) = \frac{q(t)}{C}$$


$$\Rightarrow q(t) = C E_m \sin(\omega t)$$

$$\begin{aligned} \Rightarrow \text{current } i(t) &= \frac{dq(t)}{dt} = \omega C E_m \cos(\omega t) \\ &= \omega C E_m \sin(\omega t + 90^\circ) \end{aligned}$$

9

$$\Rightarrow \phi = -90$$

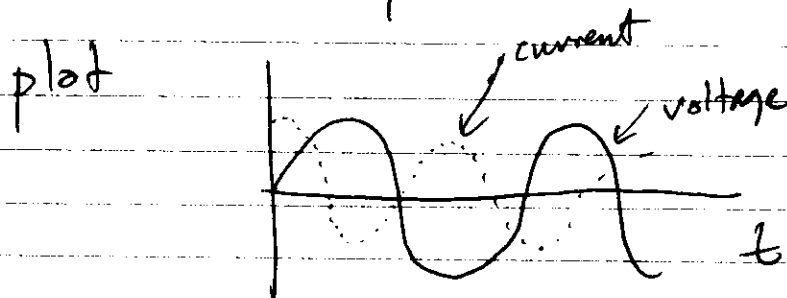
so current & voltage are out of phase by 90°



interpretation: voltage follows current
b/c hard to build up a potential difference, current goes immediately as device gets changed

Inductive load

use loop rule

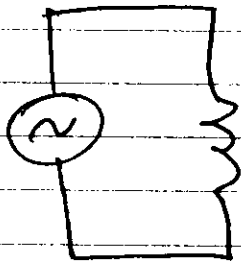

$\mathcal{E}_m \sin(\omega t)$ to get voltage

across inductor
current we get from

$$\mathcal{E}_m \sin(\omega t) = L \frac{di}{dt}$$

10

integrate to get

$$E_m \sin(\omega t) = L i$$

$$\Rightarrow -\frac{E_m}{\omega} \cos(\omega t) = L i$$

$$\begin{aligned} \Rightarrow i(t) &= -\frac{E_m}{\omega L} \cos(\omega t) \\ &= \frac{E_m}{\omega L} \sin(\omega t - 90^\circ) \end{aligned}$$

⇒ current follows voltage
b/c inductor opposes changes in
current